

# DIGITAL ELECTRONICS

## EXPERIMENT-7

*PULKIT PANDEY*

*2K19/EP/076*

**AIM:** To study the operation of 8-bit parity generator/checker; and operation of BCD to 7-segment display


**THEORY:** A parity generator is a combinational logic circuit that generates the parity bit in the transmitter. On the other hand, a circuit that checks the purity in the receiver is called a parity checker. A combined circuit or devices of parity generators and parity checkers are commonly used in digital systems to detect the single bit errors in the transmitted data word.

The sum of the data bits and parity bits can be even or odd . Even Parity, the added parity bit will make the total number of 1s uneven amounts whereas in odd parity the added parity bit will make the total number of 1s odd amounts.

The basic principle involved in the implementation of parity circuits is that the sum of odd numbers of 1s is always 1 and the sum of even numbers of 1s is always zero. Such error detecting and correction can be implemented by using Ex-OR gates (since Ex-OR gates produce zero output when there are even number of inputs).


**CIRCUIT DIAGRAM AND TRUTH TABLE:**


**8-bit parity generator/checker**

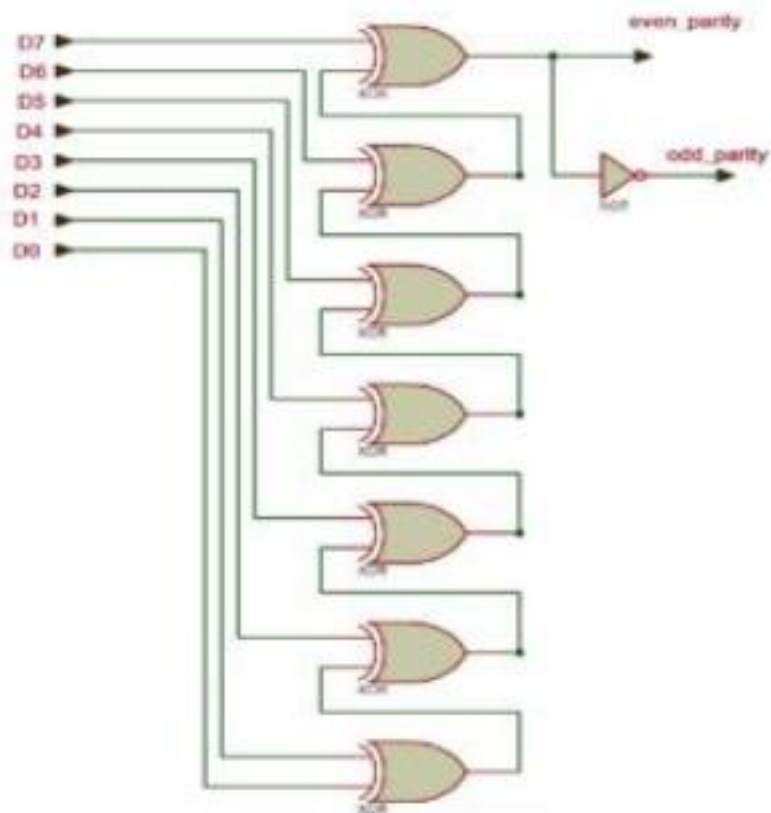

D7	D6	D5	D4	D3	D2	D1	D0	Even_parity	Odd_parity
1	0	1	1	0	0	1	0	0	1
1	1	0	0	1	0	0	0	1	0
1	1	1	1	1	0	1	1	1	0
1	0	1	1	1	1	1	0	0	1
0	0	1	0	1	0	1	0	1	0
0	1	1	1	0	1	0	1	1	0
0	1	0	1	0	0	1	1	0	1

### SOFTWARE SIMULATION:

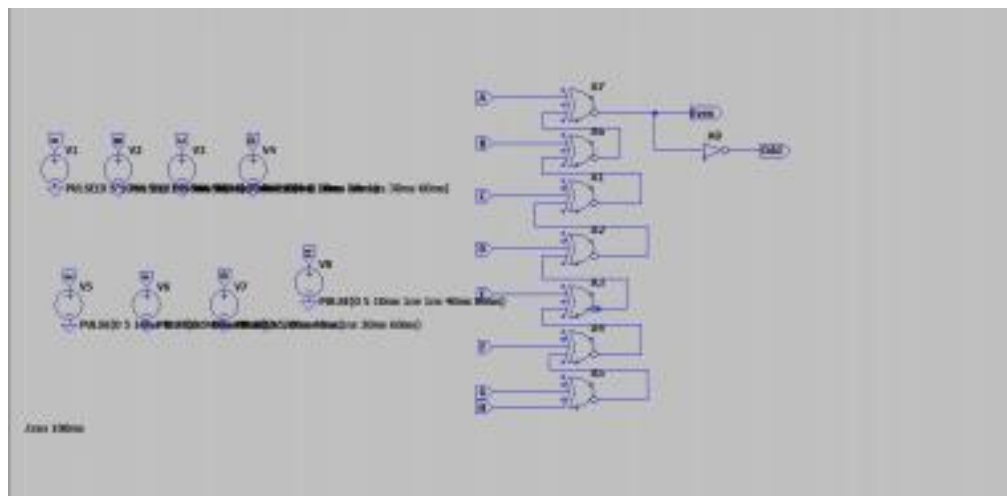

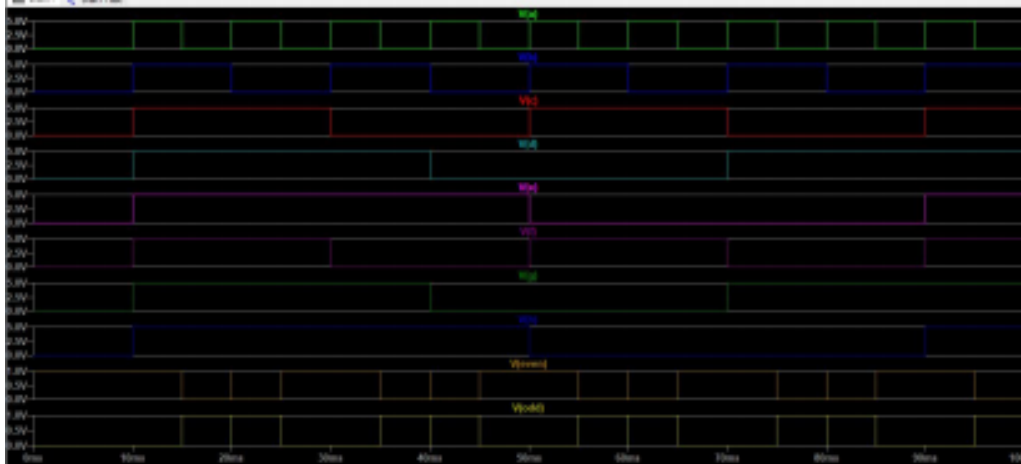

### BCD to seven segment display

In Binary Coded Decimal (BCD) encoding scheme each of the decimal numbers(0-9) is represented by its equivalent binary pattern(which is generally of 4-bits).

Whereas, Seven segment display is an electronic device which consists of seven Light Emitting Diodes (LEDs) arranged in a some definite pattern(common cathode or common anode type), which is used to display Hexadecimal numerals(in this case decimal numbers, as input is BCD i.e., 0-9).

Two types of seven segment LED display:

1. Common Cathode Type: In this type of display all cathodes of these seven LEDs are connected together to the ground or  $V_{cc}$  (hence, common cathode) and LED displays digits when some 'HIGH' signal is supplied to the individual anodes.
2. Common Anode Type: In this type of display all the anodes of these seven LEDs are connected to battery or  $+V_{cc}$  and LED displays digits when some 'LOW' signal is supplied to the individual cathodes.

### TRUTH TABLES:

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

## SOFTWARE SIMULATION

